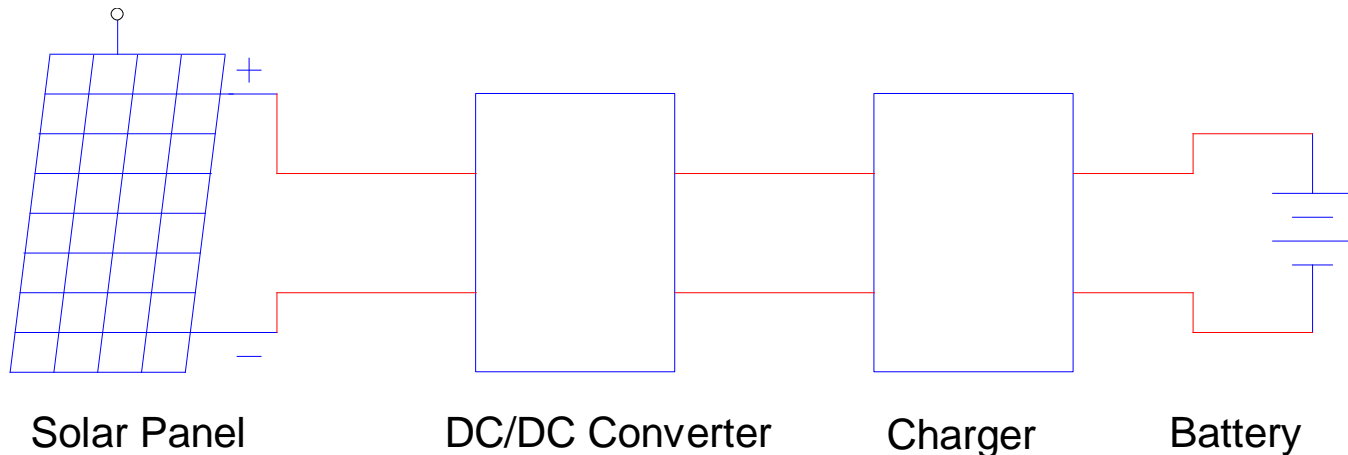


# Detailed Design

## - DC/DC Converter


### Example Design – Power Supply for Charger

- Input: 20V - 28V DC
- Output: 17V DC
- Maximum Output Current: 2A
- Isolation not required
- Operating temperature



# Detailed Design

## 1. Topology Selection

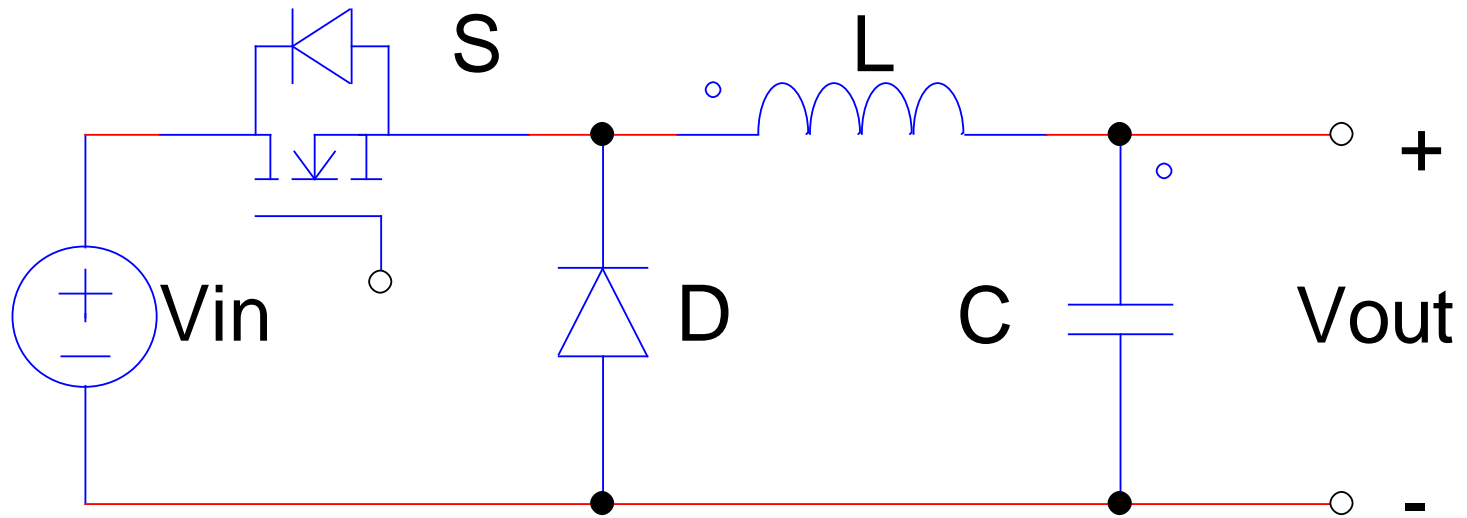

Buck Converter

Step Down

20-28V --> 17V


$$V_{out} = V_{in}D$$

For Continuous Conduction Mode  
 $D$  - Duty Cycle


# Detailed Design

## 2. Controller IC

[LM2576TV-ADJG](#)

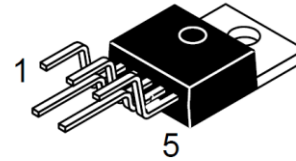


TO-220  
TV SUFFIX  
CASE 314B

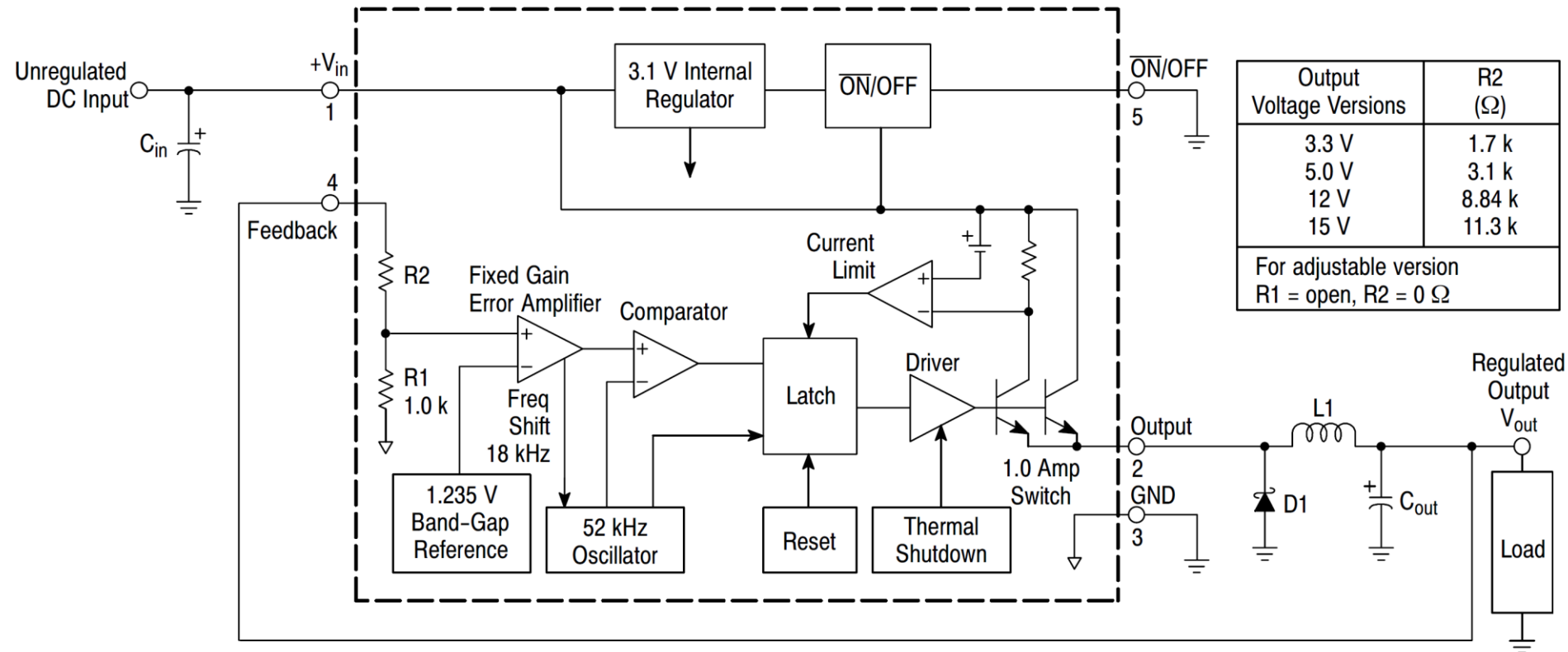

<http://www.onsemi.com/pub/Collateral/LM2576-D.PDF>

# Detailed Design

## 3. Example Circuit

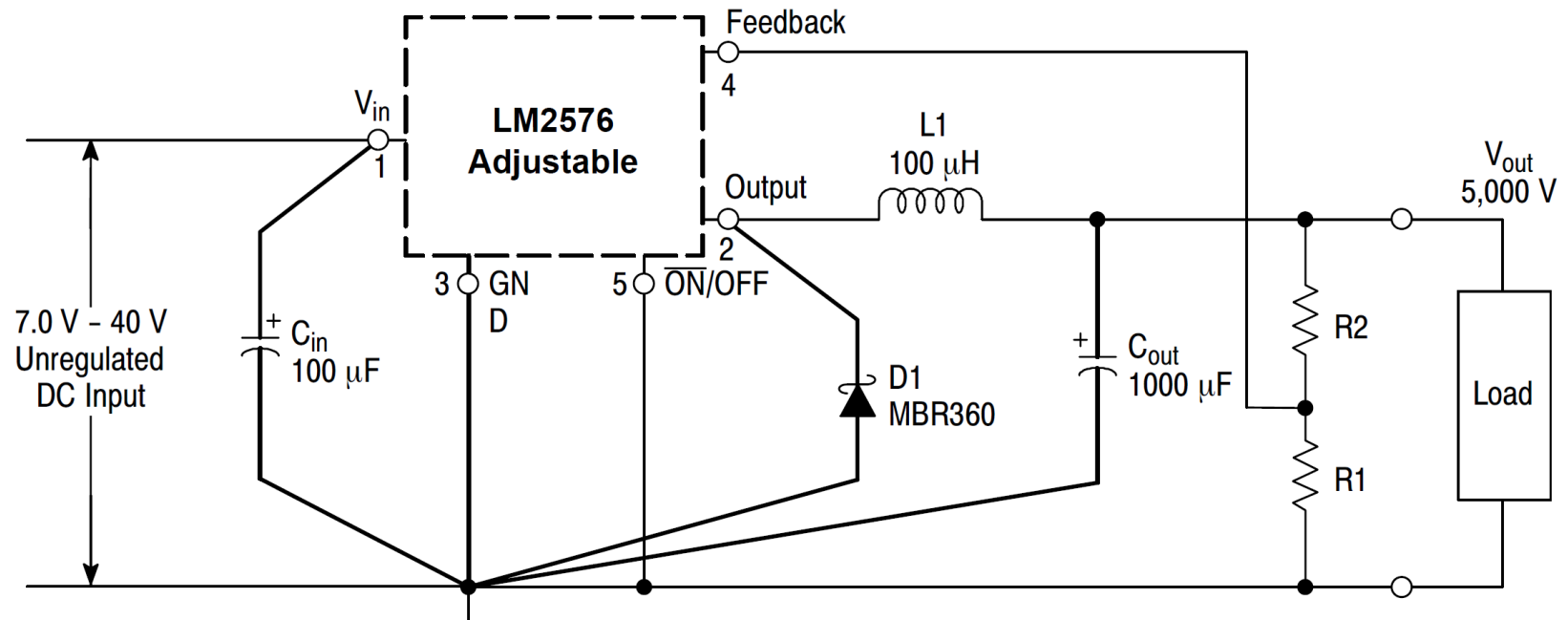

$$V_{out} = V_{ref} \left( 1.0 + \frac{R2}{R1} \right)$$

$$R2 = R1 \left( \frac{V_{out}}{V_{ref}} - 1.0 \right)$$

Where  $V_{ref} = 1.23 \text{ V}$ ,  $R1$  between  $1.0 \text{ k}$  and  $5.0 \text{ k}$

### Adjustable Output

Use voltage divider for feedback

Online tool of voltage divider calculator

[http://www.ti.com/download/kbase/volt/volt\\_div3.htm](http://www.ti.com/download/kbase/volt/volt_div3.htm)

## 4. Input Capacitor (C<sub>in</sub>) Selection

- At least 100  $\mu\text{F}$
- Electrolytic capacitor
- Low ESR
- Voltage/Current ratings
- Temperature rating
- Place the capacitor close to the regulator
- Keep the leads as short as possible



## 5. Catch Diode (D1) Selection

- Consider maximum load current  
1.5-2.5 safety factor
- Consider maximum input voltage  
1.5-2.0 safety factor
- Prefer Schottky diode (fast speed and low forward voltage drop)
- Or fast recovery diode
- Standard 60-Hz diodes (general purpose) not suitable
- Connect the diode near the IC



## 6. Inductor (L1) Selection

- Peak-to-peak inductor ripple current  
20%-30% maximum load current
- Ripple frequency 52kHz (switching frequency)
- Refer to the selection guide in the data sheet
- Check the inductor maximum current (< inductor saturation current)



## 7. Output Capacitor (C<sub>out</sub>) Selection

- Minimum capacitance (see data sheet)

$$C_{out} \geq 13,300 \frac{V_{in(max)}}{V_{out} \times L [\mu H]} [\mu F]$$

- Higher capacitance lower ripple voltage

several times larger

- Voltage rating

1.5-2.0 safety factor

- Connect the capacitor near the IC

- Recommend low ESR capacitor

however, very low ESR could lead to instability





## 8. Thermal Design

The following formula is to calculate the approximate total power dissipated by the LM2576:

$$P_D = (V_{in} \times I_Q) + d \times I_{Load} \times V_{sat}$$

where  $d$  is the duty cycle and for buck converter

$$d = \frac{t_{on}}{T} = \frac{V_O}{V_{in}},$$

$I_Q$  (quiescent current) and  $V_{sat}$  can be found in the LM2576 data sheet,

$V_{in}$  is minimum input voltage applied,

$V_O$  is the regulator output voltage,

$I_{Load}$  is the load current.

The dynamic switching losses during turn-on and turn-off can be neglected if proper type catch diode is used.



# Detailed Design

## Some WebDesign Tools

- TI WEBENCH Designer

<http://www.ti.com/design-tools/webench-power-design/power-designer.html>

- Power Supply WebDesigner

<http://www.onsemi.com/>

