

Detailed Design

- Battery Charger

- Design of an Isolated Power Supply (Option-1):
 - 120V/60Hz ac input, 15V dc output, 30W, regulated power supply
 - Electrically isolated between input and output
 - Safe to use
 - Efficient
 - Reliable
 - Economical.....
- Design of a PV-Based Battery Charger (Option-2):
 - Charger for a 12V lead-acid battery (max. 2A charging current) from a widely-variable source such as a solar panel
 - Non-isolated
 - Safe to use
 - Efficient
 - Reliable
 - Economical.....

ECE3031 Projects

ECE3031

Detailed Design

1. Design Requirements

- 12V lead-acid battery
- Maximum charging current 2A
- Optimum charging scheme (fast charging, maximizing battery capacity, maximizing battery life)
- Input 10V-28V DC
- Isolation not required
- Operating temperature




ECE3031

Detailed Design

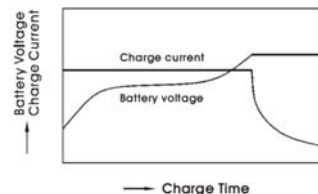2. Charging Scheme

- Constant voltage charging
2.45V/cell for cycle use; 2.275V/cell for stand-by use
- Constant current charging
0.1C-0.3C (10%-30% of rated capacity)
overcharge may occur
- 2-stage constant voltage charging
(recommended)




https://media.digikey.com/pdf/Data%20Sheets/B%20B%20Battery%20PDFs/VRLA_Man.pdf

ECE3031

Detailed Design

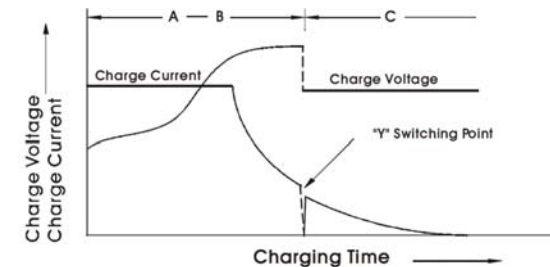2. Charging Scheme

2-stage constant voltage charging with limited current



- Voltage 2.45V/cell
 - Limited current, e.g. around 0.3C (2.1A for 7Ah battery)
 - Constant 2.45V/cell until current decreases to the switching point
- Voltage 2.275V/cell (float/stand-by charging)

ECE3031

Detailed Design

3. Charger IC Selection

Considerations:

- Battery type (lead-acid)
- Voltage level (12V, 6 cell)
- Charging control (multi-stage charging)
- Availability on the market (digkey.ca)
- IC packaging/footprint (easy for soldering/connecting)

Selections:


- BQ24450 (SOIC packaging)
- UC2906/UC3906 (has DIP package UC2906N)

ECE3031

Detailed Design

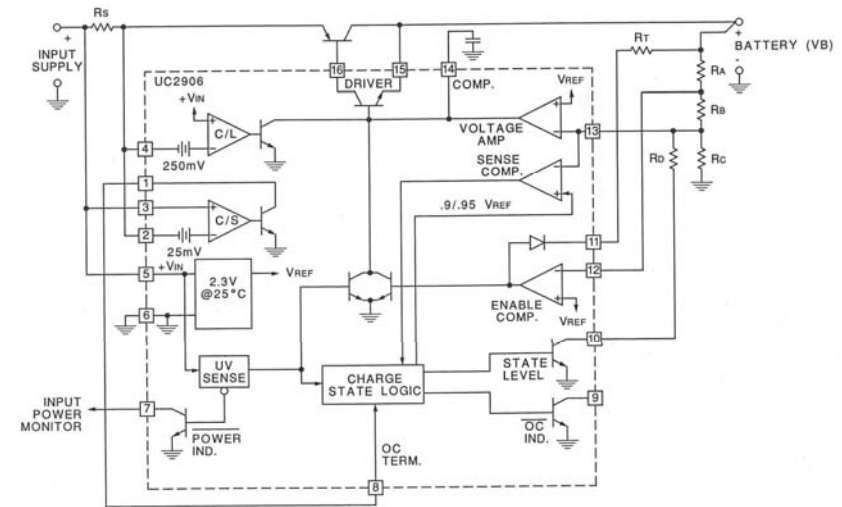4. Charger IC UC2906

<http://www.ti.com/lit/ds/symlink/uc2906.pdf>





Typical circuit diagram for 2-stage float charger

ECE3031

Detailed Design


4. Charger IC UC2906

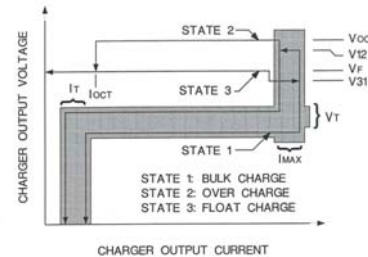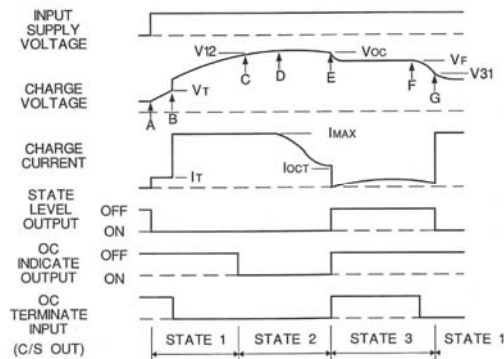

ECE3031

Detailed Design

4. Charger IC UC2906

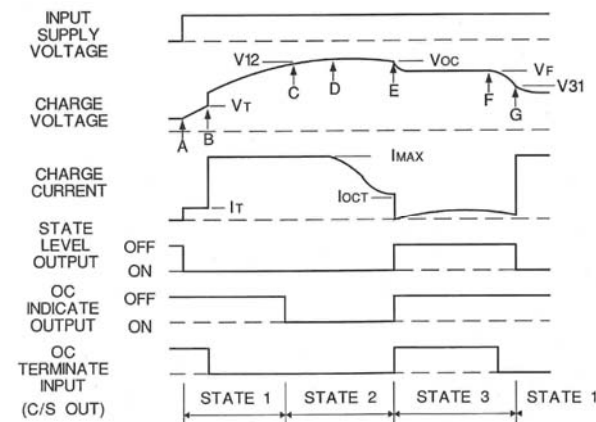

V_F	2.275V/cell
V_{OC}	2.45V/cell
V_T	1.75V/cell
I_{MAX}	0.3C
I_T	<25mA

ECE3031

Detailed Design

4. Charger IC UC2906

$$\begin{aligned}V_F &= 2.275\text{V/cell} \\V_{OC} &= 2.45\text{V/cell} \\V_T &= 1.75\text{V/cell} \\I_{MAX} &= 0.3\text{C} \\I_T &< 25\text{mA}\end{aligned}$$

Design Procedure

1) Pick divider current, I_D . Recommended value is $50\mu\text{A}$ to $100\mu\text{A}$.

$$2) R_C = 2.3\text{V} / I_D$$

$$3) R_A + R_B = R_{SUM} = (V_F - 2.3\text{V}) / I_D$$

$$4) R_D = 2.3\text{V} \cdot R_{SUM} / (V_{OC} - V_F)$$

$$5) R_A = (R_{SUM} + R_X)(1 - 2.3\text{V} / V_T)$$

WHERE: $R_X = R_C \cdot R_D / (R_C + R_D)$

$$6) R_B = R_{SUM} - R_A$$

$$7) R_S = 0.25\text{V} / I_{MAX}$$

$$8) R_T = (V_{IN} - V_T - 2.5\text{V}) / I_T$$

$$9) I_{OCT} = \frac{I_{MAX}}{10}$$

Note: $V_{12} = 0.95 V_{OC}$,
 $V_{31} = 0.90 V_F$.

ECE3031

Detailed Design

5. External Pass Transistor Selection

Considerations:

- Common-Emitter PNP or Darlington
- Voltage rating
- Current rating
- Minimum delta voltage
- Maximum power dissipation
- Thermal design

ECE3031