


## What is a Power Supply?

- Power converters – change electrical quantity from one form to another:
  - AC-DC (rectifier)
  - DC-DC (chopper)
  - DC-AC (inverter)
  - AC-AC (ac voltage controller, cyclo-converter)
- A power supply may consist of a combination of power converters to provide a power source for a load. Almost all electronic equipment need a power supply
- In addition to the need for a certain power rating of a voltage level, there could be other requirements, such as regulated output, and isolation
- Attributes (features) of the power supply you are to design: safe (to use); efficient; reliable; and economical. And other attributes if you would like to add

ECE3031

## Various Power Supplies


- Isolated (electrical separation between input and output) v.s. non-isolated
- Open frame v.s. closed frame (closed box)

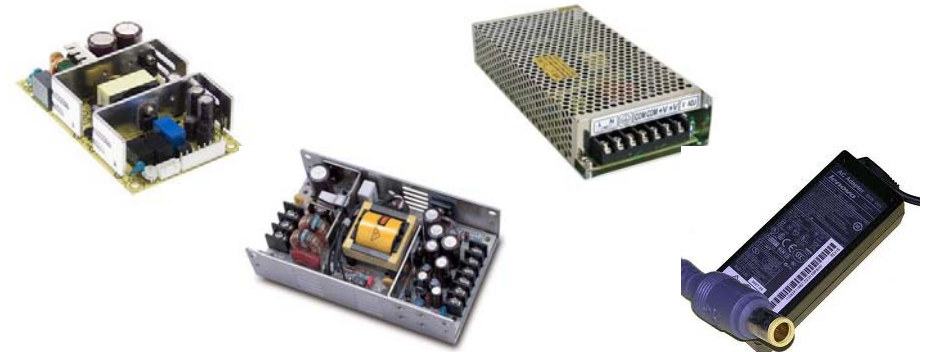

ECE3031
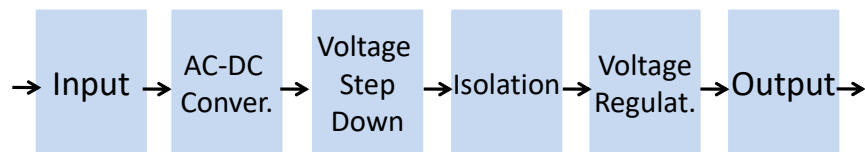
## Functional Structure of a Power Supply

- Input: 120V, ac (60Hz)
- Output: 15V, 30W, dc, regulated (constant volt), isolated
- Functions: ac-dc conversion; isolation; voltage step down; voltage regulation; input; output.



- The structure of the design may be different

ECE3031

## Power Supply Specifications

- Input voltage range (the maximum voltage and minimum voltage limits that the power supply can accept while still has rated output)
- Output voltage – nominal voltage (fixed, or variable in a range, or multiple values)
- Efficiency:  $\eta = P_{out} / P_{in} \times 100\%$ ;  $P_{out} = P_{in} - P_{loss}$
- Line regulation:  $VR_{Line} = (V_{out@Vinmax} - V_{out@Vinmin}) / V_{out@rated} \times 100\%$
- Load regulation:  $VR_{Load} = (V_{out@maxLoad} - V_{out@minLoad}) / V_{out@rated} \times 100\%$
- Other features: remote sensing (voltage regulate at the load site instead of the output terminals)
- Cooling and thermal management: natural, force air (fan), conduction
- Protection functions: over-current, over-temperature, auto-restart
- Standards and certification

ECE3031

## Types of Power Supply

- Unregulated  
transformer + rectifier + filter
- Linear regulated  
Zener diode  
Linear regulator ICs
- Switching regulated  
Switched-mode power supply
- Others

ECE3031

## Unregulated Power Supply

- Unregulated AC-DC  
transformer + rectifier + filter
  - Simple
  - Flexible
  - Isolated
- Unregulated DC-DC  
think of a voltage divider


ECE3031

## Linear Regulated

- Zener diode (shunt regulator)
- Zener diode + Emitter follower (series regulator)
- Linear regulator ICs
  - Fixed voltage
  - Variable voltage

ECE3031

## Linear Regulator

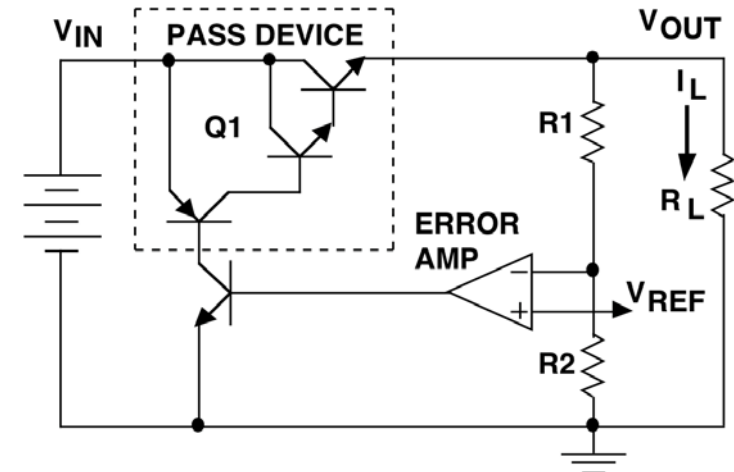

ECE3031

## Switching Regulated (Switched-mode power supply)

- Non-isolated:
  - Buck converter
  - Boost converter
  - Buck-boost converter
  - ...
- Isolated:
  - Flyback converter
  - Forward converter
  - ...

ECE3031

## Switched-mode power supply

- PWM – Pulse Width Modulation
- Switching Frequency
- Duty Cycle Ratio
- CCM – Continuous Conduction Mode
- DCM – Discontinuous Conduction Mode
- Freewheeling Diode
- MOSFET
  - metal-oxide-semiconductor field-effect transistor

ECE3031

## Switched-mode power supply

### Principles of steady-state analysis:

- ✓ Inductor volt-second balance  
integral/average voltage = 0
- ✓ Capacitor charge (amp-second) balance  
integral/average current = 0

ECE3031

Buck converter:  $V_o = V_s D$

Boost converter:  $V_o = \frac{V_s}{1 - D}$

CCM Mode

Buck-boost and Ćuk converters:  $V_o = -V_s \left( \frac{D}{1 - D} \right)$

SEPIC:  $V_o = V_s \left( \frac{D}{1 - D} \right)$


Flyback converter:  $V_o = V_s \left( \frac{D}{1 - D} \right) \left( \frac{N_2}{N_1} \right)$

Forward converter:  $V_o = V_s D \left( \frac{N_2}{N_1} \right)$

3031

# Switched-mode power supply

Example: Single-output Flyback Circuit Diagram

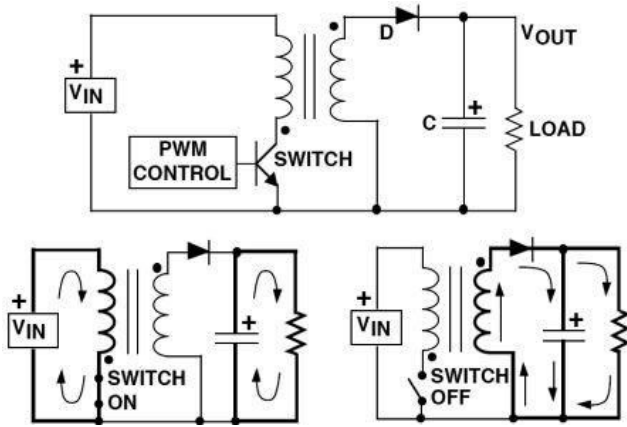


ECE3031

# Switched-mode power supply

A Typical Application from Datasheet:

[https://ac-dc.power.com/sites/default/files/product-docs/topswitch-jx\\_family\\_datasheet.pdf?download=1](https://ac-dc.power.com/sites/default/files/product-docs/topswitch-jx_family_datasheet.pdf?download=1)

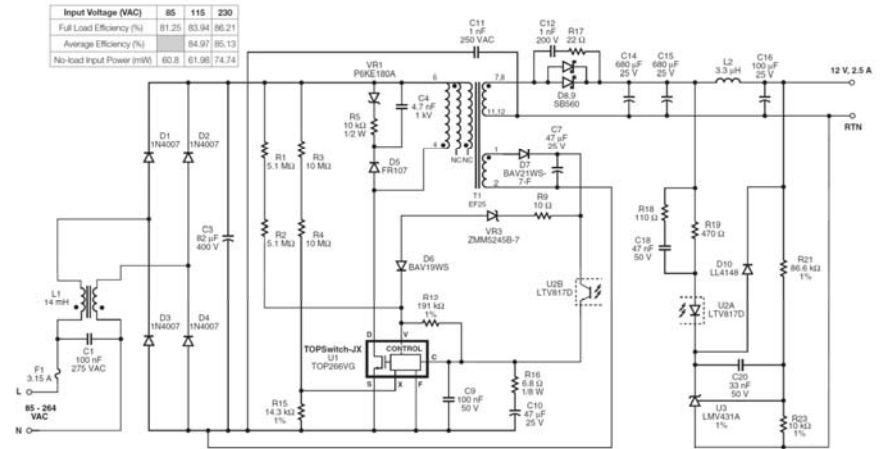

ECE3031