

6. Circuit Analysis

MTVW 25-Feb-13

Objectives

1. To compare the analysis of series-parallel circuits with experimental measurements.
 2. To investigate the effect of “open” and “short” circuits
 3. To use Superposition and Mesh Current Analysis to aid in determining circuit values.
-

Equipment

1. 5 V and -5 VDC power supplies (these are in the same case),
 2. One SPST switch,
 3. 402 Ω , 90 Ω and 150 Ω carbon resistors,
-

Preparation

1. Analyze the series-parallel circuit in Figure 1 with the switch open and compute the currents, I_0 , I_1 , I_2 , I_3 , and I_5 and the voltages, V_{AC} , V_{BA} , V_{CB} , and V_{DC} . Enter the computed values into Table 4 a). Using the computed values in Table 4 a) complete Table 4 c).
2. Analyze the series-parallel circuit in Figure 1 with the switch closed and compute the currents, I_0 , I_1 , I_2 , I_3 , and I_5 and the voltages, V_{AC} , V_{BA} , V_{CB} , and V_{DC} . Enter the computed values into Table 5 a). Using the computed values in Table 5 a) complete Table 5 c).
3. Analyze the circuit of Figure 2 using superposition to determine the voltage across R_3 . Space has been provided for your analysis.
4. Analyze the circuit of Figure 2 using Mesh Current Analysis to determine the voltage across R_3 . Space has been provided for your analysis.

Experiment

1. Analysis of a Resistive Circuit using Ohms Law, KVL, and KCL

Consider the series-parallel circuit in Figure 1. Table 4 a), Table 4 c), Table 5 a) and Table 5 c), will have been completed as preparation before attending the lab.

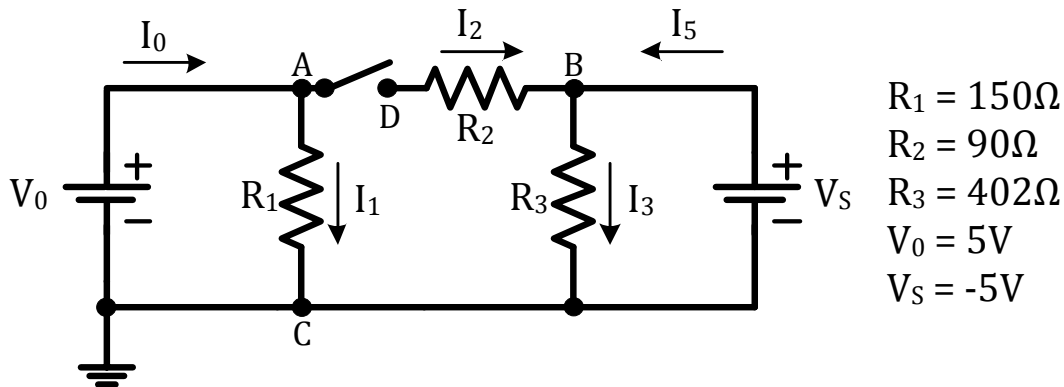


Figure 1: Series-parallel circuit to be analyzed and constructed.

Before wiring up the circuit use the multimeter to measure the resistances of R_1 , R_2 and R_3 and enter the measured values into Table 4 b) and Table 5 b). Wire up the circuit and record the measured currents and voltages in Table 4 b) when the switch is open; and into Table 5 b) when the switch is closed.

Verify Ohm's Law for each of the resistors, KCL at nodes A & B, and KVL (around one of the loops) by completing Table 4 c) and Table 5 c) using measured voltages and currents.

2. Analysis of a Resistive Circuit using Superposition and Mesh Current Analysis.

Wire up the circuit of Figure 2 and measure V_{R3} . Compare with your calculated value from your Superposition and Mesh Current Analysis.

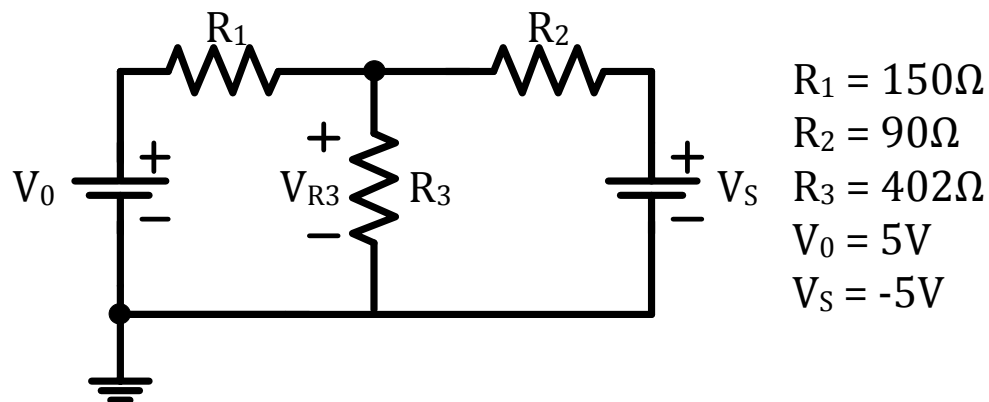


Figure 2: Mesh Loop and Superposition Analysis Circuit.

6. WORKSHEET Name: _____ Section: _____ ID#: _____

Table 4 a). Analysis Results (completed as lab preparation)										
S-Open	I_0	I_1	I_2	I_3		I_5	V_{AC}	V_{BA}	V_{CB}	V_{DC}
S-Open										
Table 4 b). Measured Values										
S-Open	I_0	I_1	I_2	I_3		I_5	V_{AC}	V_{BA}	V_{CB}	V_{DC}
S-Open										
Resistances	R_1		R_2		R_3					
Resistances										
Table 4 c). Computed from Analysis Results (as lab preparation) in Table 4 a)										
S-Open	V_{AC}/I_1		V_{AB}/I_2		V_{BC}/I_3		$V_{AC} + V_{DA} + V_{BD} + V_{CB}$			
S-Open										
s-Open	$I_2 - I_3 + I_5$		$I_0 - I_1 - I_2$							
S-Open										
Table 4 d). Computed from Measured Results in Table 5 b)										
S-Open	V_{AC}/I_1		V_{AB}/I_2		V_{BC}/I_3		$V_{AC} + V_{DA} + V_{BD} + V_{CB}$			
S-Open										
S-Open	$I_2 - I_3 + I_5$		$I_0 - I_1 - I_2$							
S-Open										

Table 5 a). Analysis Results (completed as lab preparation)										
S-Closed	I_0	I_1	I_2	I_3		I_5	V_{AC}	V_{BA}	V_{CB}	V_{DC}
S-Closed										
Table 5 b). Measured Values										
S-Closed	I_0	I_1	I_2	I_3		I_5	V_{AC}	V_{BA}	V_{CB}	V_{DC}
S-Closed										
Resistances	R_1		R_2		R_3					
Resistances										
Table 5 c). Computed from Analysis Results (as lab preparation) in Table 5 a)										
S-Closed	V_{AC}/I_1		V_{AB}/I_2		V_{BC}/I_3		$V_{AC} + V_{DA} + V_{BD} + V_{CB}$			
S-Closed										
S-Closed	$I_2 - I_3 + I_5$		$I_0 - I_1 - I_2$							
S-Closed										
Table 5 d). Computed from Measured Results in Table 5 b)										
S-Closed	V_{AC}/I_1		V_{AB}/I_2		V_{BC}/I_3		$V_{AC} + V_{DA} + V_{BD} + V_{CB}$			
S-Closed										
S-Closed	$I_2 - I_3 + I_5$		$I_0 - I_1 - I_2$							
S-Closed										

***Indicate all assumed voltage polarities and current directions**

Superposition Analysis of the circuit of Figure 2:

***Indicate all assumed voltage polarities and current directions**

Mesh Current Analysis of the circuit of Figure 2:

Comparison: