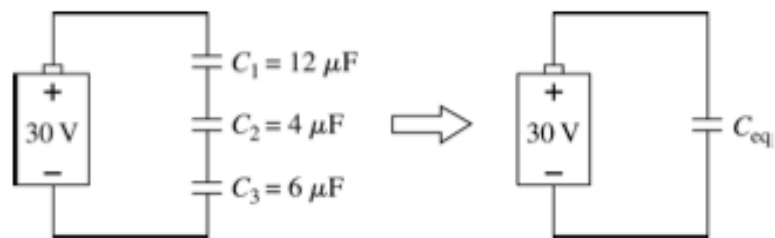


## Exercises and Problems from chapter 29

**29.53. Model:** Assume that the battery is ideal.**Visualize:**

The pictorial representation shows the equivalent capacitance of the three capacitors.

**Solve:** Because  $C_1$ ,  $C_2$ , and  $C_3$  are in series,

$$\frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} = \frac{1}{12 \mu\text{F}} + \frac{1}{4 \mu\text{F}} + \frac{1}{6 \mu\text{F}} = \frac{1}{2} (\mu\text{F})^{-1} \Rightarrow C_{\text{eq}} = 2 \mu\text{F}$$

A potential difference of  $\Delta V_C = \mathcal{E} = 30 \text{ V}$  across a capacitor of equivalent capacitance  $2 \mu\text{F}$  produces a charge  $Q = C_{\text{eq}} \Delta V_C = (2 \mu\text{F})(30 \text{ V}) = 60 \mu\text{C}$ . Because  $C_{\text{eq}}$  is a combination of three series capacitors,  $Q_1 = Q_2 = Q_3 = 60 \mu\text{C}$ .


We are now able to find the potential difference across each capacitor:

$$\Delta V_1 = \frac{Q_1}{C_1} = \frac{60 \mu\text{C}}{12 \mu\text{F}} = 5.0 \text{ V} \quad \Delta V_2 = \frac{Q_2}{C_2} = \frac{60 \mu\text{C}}{4 \mu\text{F}} = 15 \text{ V} \quad \Delta V_3 = \frac{Q_3}{C_3} = \frac{60 \mu\text{C}}{6 \mu\text{F}} = 10 \text{ V}.$$

**Assess:**  $\Delta V_1 + \Delta V_2 + \Delta V_3 = 30 \text{ V} = \Delta V_{\text{bat}}$ , as it should.

**29.55. Model:** Assume the battery is an ideal battery.

**Visualize:**

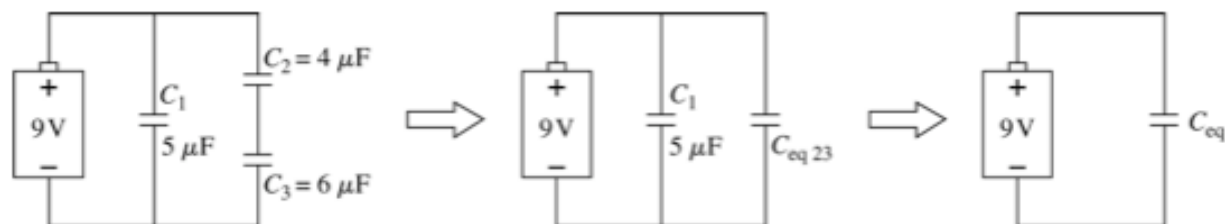

The pictorial representation shows how to find the equivalent capacitance of the three capacitors shown in the figure.

**Solve:** Because  $C_2$  and  $C_3$  are in series,

$$\frac{1}{C_{eq\ 23}} = \frac{1}{C_2} + \frac{1}{C_3} = \frac{1}{4\ \mu\text{F}} + \frac{1}{6\ \mu\text{F}} = \frac{10}{24}(\mu\text{F})^{-1} \Rightarrow C_{eq\ 23} = \frac{12}{5}\ \mu\text{F} = 2.4\ \mu\text{F}$$

$C_{eq\ 23}$  and  $C_1$  are in parallel, so

$$C_{eq} = C_{eq\ 23} + C_1 = 2.4\ \mu\text{F} + 5\ \mu\text{F} = 7.4\ \mu\text{F}$$

A potential difference of  $\Delta V_C = 9\ \text{V}$  across a capacitor of equivalent capacitance  $7.4\ \mu\text{F}$  produces a charge

$$Q = C_{eq}\Delta V_C = \left(\frac{37}{5}\ \mu\text{F}\right)(9\ \text{V}) = \frac{333}{5}\ \mu\text{C}$$

Because  $C_{eq}$  is a parallel combination of  $C_1$  and  $C_{eq\ 23}$ , these capacitors have  $\Delta V_1 = \Delta V_{eq\ 23} = \Delta V_C = 9\ \text{V}$ . Thus the charges on these two capacitors are

$$Q_1 = (5\ \mu\text{F})(9\ \text{V}) = 45\ \mu\text{C} \quad Q_{eq\ 23} = (2.4\ \mu\text{F})(9\ \text{V}) = 21.6\ \mu\text{C}$$

Because  $Q_{eq\ 23}$  is due to a series combination of  $C_2$  and  $C_3$ ,  $Q_2 = Q_3 = 21.6\ \mu\text{C}$ . This means

$$\Delta V_2 = \frac{Q_2}{C_2} = \frac{21.6\ \mu\text{C}}{4\ \mu\text{F}} = 5.4\ \text{V} \quad \Delta V_3 = \frac{Q_3}{C_3} = \frac{21.6\ \mu\text{C}}{6\ \mu\text{F}} = 3.6\ \text{V}$$

Thus, to two significant figures,  $Q_1 = 45\ \mu\text{C}$ ,  $V_1 = 9\ \text{V}$ ;  $Q_2 = 22\ \mu\text{C}$ ,  $V_2 = 5.4\ \text{V}$ ; and  $Q_3 = 22\ \mu\text{C}$ ,  $V_3 = 3.6\ \text{V}$ .

**29.59. Model:** Assume the battery is ideal.

**Visualize:** Please refer to Figure P29.59. While the switch is in position A, the capacitors  $C_2$  and  $C_3$  are uncharged. When the switch is placed in position B, the charged capacitor  $C_1$  is connected to  $C_2$  and  $C_3$ .  $C_2$  and  $C_3$  are connected in series to form an equivalent capacitor  $C_{eq\ 23}$ .

**Solve:** While the switch is in position A, a potential difference of  $V_1 = 100\ \text{V}$  across  $C_1$  charges it to

$$Q_1 = C_1 V_1 = (15\ \mu\text{F})(100\ \text{V}) = 1500\ \mu\text{C}$$

When the switch is moved to position B, this initial charge  $Q_1$  is redistributed. The charge  $Q'_1$  goes on  $C_1$  and the charge  $Q_{eq\ 23}$  goes on  $C_{eq\ 23}$ . The voltage across  $C_1$  and  $C_{eq\ 23}$  is the same and  $Q'_1 + Q_{eq\ 23} = Q_1 = 1500\ \mu\text{C}$ . Combining these two conditions, we get

$$\frac{Q'_1}{C_1} = \frac{Q_{eq\ 23}}{C_{eq\ 23}} \Rightarrow \frac{1500\ \mu\text{C} - Q_{eq\ 23}}{C_1} = \frac{Q_{eq\ 23}}{C_{eq\ 23}}$$

Since  $C_{eq\ 23} = \left(\frac{1}{20\ \mu\text{F}} + \frac{1}{30\ \mu\text{F}}\right)^{-1} = 12\ \mu\text{F}$ , we can rewrite this equation as

$$\frac{1500\ \mu\text{C} - Q_{eq\ 23}}{15\ \mu\text{F}} = \frac{Q_{eq\ 23}}{12\ \mu\text{F}} \Rightarrow Q_{eq\ 23} = 0.67\ \text{mC} \Rightarrow Q'_1 = Q_1 - Q_{eq\ 23} = 1.500\ \text{mC} - 0.67\ \text{mC} = 0.83\ \text{mC}$$

Having found the charge  $Q_{eq\ 23}$ , it is easy to see that  $Q_2 = Q_3 = 0.67\ \text{mC}$  because  $C_{eq\ 23}$  is a series combination of  $C_2$  and  $C_3$ . Thus,

$$\Delta V_1 = \frac{Q'_1}{C_1} = \frac{830\ \mu\text{C}}{15\ \mu\text{F}} = 55\ \text{V} \quad \Delta V_2 = \frac{Q_2}{C_2} = \frac{670\ \mu\text{C}}{20\ \mu\text{F}} = 34\ \text{V} \quad \Delta V_3 = \frac{Q_3}{C_3} = \frac{670\ \mu\text{C}}{30\ \mu\text{F}} = 22\ \text{V}$$

### Conceptual Questions from chapter 30

**30.9.** (a)  $I_1 = I_2$ . Due to conservation of current, the current everywhere in the wire is the same. The number of charges passing per unit time must be the same in wires 1 and 2.

(b) By definition,  $J_1 = \frac{I}{A_1}$  and  $J_2 = \frac{I}{A_2}$ . Since  $A_1 < A_2$ ,  $J_1 > J_2$ .

(c) Since  $\sigma_1 = \sigma_2 = \sigma$ ,  $E_1 = \frac{J_1}{\sigma}$  and  $E_2 = \frac{J_2}{\sigma}$ . So  $E_1 > E_2$ .

(d) We have  $J = nev_d$ . Since  $J_1 > J_2$ ,  $(v_d)_1 > (v_d)_2$ .

**30.11.**  $R_d > R_a = R_e > R_c > R_b$ . Calculate  $R = \frac{\rho L}{A}$ :

$$R_a = \frac{\rho L}{\pi r^2}$$

$$R_c = \frac{\rho(2L)}{(\pi)(2r)^2} = \frac{1}{2}R_a$$

$$R_b = \frac{\rho L}{(\pi)(2r)^2} = \frac{1}{4}R_a$$

$$R_d = \frac{\rho(2L)}{\pi r^2} = 2R_a$$

$$R_e = \frac{\rho(4L)}{(\pi)(2r)^2} = R_a$$

### Exercises and Problems from chapter 30

**30.11. Solve:** From Equation 30.13, the current in the wire is

$$I = JA = (7.50 \times 10^5 \text{ A/m}^2)(2.5 \times 10^{-6} \text{ m} \times 75 \times 10^{-6} \text{ m}) = 0.141 \text{ mA}$$

The charge that flows in 15 min is the current times the time.

$$Q = I\Delta t = (0.141 \text{ A})(900 \text{ s}) = 127 \text{ C} \approx 130 \text{ C}$$

**30.21. Solve:** From Equations 30.17 and 30.18, the resistivity is

$$\rho = \frac{E}{J} = \frac{E}{I/A} = \frac{EA}{I} = \frac{E\pi r^2}{I} = \frac{(0.085 \text{ V/m})\pi(1.5 \times 10^{-3} \text{ m})^2}{12 \text{ A}} = 5.0 \times 10^{-8} \Omega \text{ m}$$

**30.27. Solve:** (a) Resistivity depends only on the type of material, not the geometry of the wire. Wires 1 and 2 are made of the same material, so  $\rho_2 = \rho_1$  and thus  $\rho_2/\rho_1 = 1.00$ .

(b) The resistance of a wire of length  $L$  and radius  $r$  is given by Equation 30.22:

$$R = \frac{\rho L}{A} = \frac{\rho L}{\pi r^2}$$

Because the two wires have the same resistivity,

$$\frac{R_2}{R_1} = \frac{\rho L_2 / \pi r_2^2}{\rho L_1 / \pi r_1^2} = \left(\frac{r_1}{r_2}\right)^2 \frac{L_2}{L_1} = \left(\frac{1}{2}\right)^2 \frac{2}{1} = \frac{1}{2} = 0.50$$

**30.41. Solve:** (a) The current associated with the moving film is the rate at which the charge on the film moves past a certain point. The tangential speed of the film is

$$v = \omega r = (90 \text{ rpm})(4.0 \text{ cm}) = 90 \frac{\text{rev}}{\text{min}} \times \frac{1 \text{ min}}{60 \text{ s}} \times \frac{2\pi \text{ rad}}{1 \text{ rev}} \times 1.0 \text{ cm} = 9.425 \text{ cm/s}$$

In 1.0 s the film moves a distance of 9.425 cm. This means the area of the film that moves to the right in 1.0 s is  $(9.425 \text{ cm})(4.0 \text{ cm}) = 37.7 \text{ cm}^2$ . The amount of charge that passes to the right in 1.0 s is

$$Q = (37.7 \text{ cm}^2)(-2.0 \times 10^{-9} \text{ C/cm}^2) = -75.4 \times 10^{-9} \text{ C}$$

Since  $I = Q/\Delta t$ , we have

$$I = \frac{|-(75.4 \times 10^{-9} \text{ C})|}{1 \text{ s}} = 75.4 \text{ nA}$$

The current is 75 nA.

(b) Having found the current in part (a), we can once again use  $I = Q/\Delta t$  to obtain  $\Delta t$ :

$$\Delta t = \frac{Q}{I} = \frac{|-10 \times 10^{-6} \text{ C}|}{75.4 \times 10^{-9} \text{ A}} = 133 \text{ s} \approx 130 \text{ s}$$

**30.46. Solve:** The total charge in the battery is

$$Q = I\Delta t = (90 \text{ A})(3600 \text{ s}) = 3.2 \times 10^5 \text{ C}$$