

ECE1813 Fall 2015 Assignment #6 Solutions

Exercises and Problems from chapter 30

30.59. Solve: From Equation 30.17 and Table 30.2, the electric field is

$$E = \frac{J}{\sigma} = \frac{I}{\sigma A} = \frac{5.0 \text{ A}}{(1.0 \times 10^7 \text{ } \Omega^{-1} \text{ m}^{-1}) \pi (1.0 \times 10^{-3} \text{ m})^2} = 0.16 \text{ V/m}$$

30.61. Model: Assume the resistors are ohmic.

Solve: The potential difference across the resistor on the left is \mathcal{E} , so the current in it is $I = \mathcal{E}/R$. The potential difference across the resistor on the right is $2\mathcal{E}$. For the current to be the same in that resistor, the resistance must be twice as much, so that $I = 2\mathcal{E}/(2R)$. Therefore, the resistance of the resistor on the right is $2R$.

Assess: The two resistors are neither in parallel nor in series.

30.65. Model: The wire is uniform. The electric field in the wire is the negative of the slope of the V vs. s curve.

Solve: The electric field in the wire is

$$E = -\frac{\Delta V}{\Delta s} = -\frac{(3.0 \text{ V} - 0.0 \text{ V})}{(0.30 \text{ m} - 0.0 \text{ m})} = -10 \text{ V/m}$$

The negative sign indicates the electric field direction is along the negative s direction, and is not needed to find current density. From Table 30.2, the conductivity of tungsten is $\sigma = 1.8 \times 10^7 \text{ } \Omega^{-1} \text{ m}^{-1}$. Thus the current density in the wire is

$$J = \sigma E = (1.8 \times 10^7 \text{ } \Omega^{-1} \text{ m}^{-1})(10 \text{ V/m}) = 1.8 \times 10^8 \text{ A/m}^2$$


31.4. R_1 dissipates more power, since $P = I^2 R$ and the same current flows through each resistor.

31.5. R_2 dissipates more power, since $P = (\Delta V)^2 / R$ and both resistors have the same potential drop ΔV because they are connected in parallel.

Conceptual Questions from chapter 31

Exercises and Problems from chapter 31

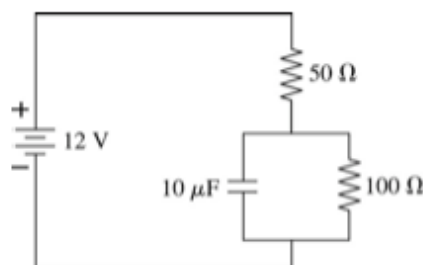31.2. Solve: In Figure EX31.2, the positive terminal of the battery is connected to the $50\ \Omega$ resistor, whose other end is connected to the $100\ \Omega$ resistor and the capacitor, which are in parallel. Thus, we have a resistor connected in series with a parallel combination of a resistor and a capacitor.



31.5. Model: The batteries and the connecting wires are ideal.

Visualize: Please refer to Figure EX31.5.


Solve: (a) Choose the current I to be in the clockwise direction. If I ends up being a positive number, then the current really does flow in this direction. If I is negative, the current really flows counterclockwise. There are no junctions, so I is the same for all elements in the circuit. With the 9 V battery labeled 1 and the 6 V battery labeled 2, Kirchhoff's loop law gives

$$\sum \Delta V_i = \Delta V_{\text{bat } 1} + \Delta V_R + \Delta V_{\text{bat } 2} = +\mathcal{E}_1 - IR - \mathcal{E}_2 = 0$$

$$I = \frac{\mathcal{E}_1 - \mathcal{E}_2}{R} = \frac{9\text{ V} - 18\text{ V}}{10\ \Omega} = -0.9\text{ A}$$

Note the signs: Potential is gained in battery 1, but potential is lost both in the resistor and in battery 2. Because I is negative, we can say that $I = 0.9\text{ A}$ and flows from right to left through the resistor.

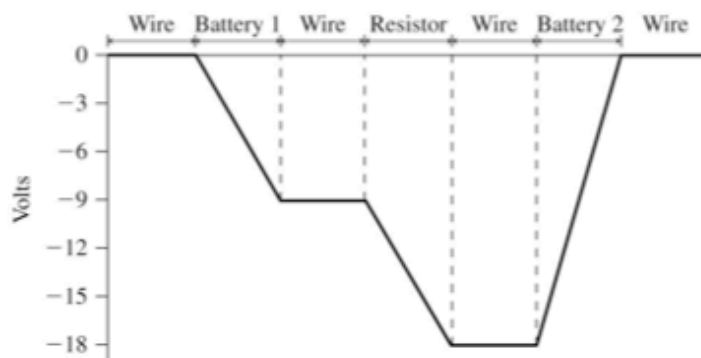(b) In the graph below, we start at the lower-left corner of the circuit and travel clockwise around the circuit (i.e., against the current). We start by losing 9 V going through battery 1, then loss $\Delta V_R = -IR = 9\text{ V}$ going through the resistor. We then gain 18 V going through battery 2. The final potential is the same as the initial potential, as required.



31.12. Solve: The cost of running the waterbed 25% of the time for a year is

$$(0.25)(450\text{ W})(365\text{ days}) \left(\frac{24\text{ hr}}{\text{day}} \right) \left(\frac{\text{kW}}{1000\text{ W}} \right) \left(\frac{\$0.12}{\text{kW hr}} \right) = \$118$$

To two significant figures, the cost is \$120.

31.17. Model: Assume ideal connecting wires but not an ideal battery.

Visualize: The circuit for an ideal battery is the same as the circuit in Figure EX31.17, except that the $1\ \Omega$ resistor is not present.

Solve: In the case of an ideal battery, we have a battery with $\mathcal{E} = 15\text{ V}$ connected to two series resistors of $10\ \Omega$ and $20\ \Omega$ resistance. Because the equivalent resistance is $R_{\text{eq}} = 10\ \Omega + 20\ \Omega = 30\ \Omega$ and the potential difference across R_{eq} is 15 V , the current in the circuit is

$$I = \frac{\Delta V}{R_{\text{eq}}} = \frac{\mathcal{E}}{R_{\text{eq}}} = \frac{15\text{ V}}{30\ \Omega} = 0.50\text{ A}$$

The potential difference across the $20\ \Omega$ resistor is

$$\Delta V_{20} = IR = (0.50\text{ A})(20\ \Omega) = 10\text{ V}$$

In the case of a real battery, we have a battery with $\mathcal{E} = 15\text{ V}$ connected to three series resistors: $10\ \Omega$, $20\ \Omega$, and an internal resistance of $1\ \Omega$. Now the equivalent resistance is

$$R'_{\text{eq}} = 10\ \Omega + 20\ \Omega + 1\ \Omega = 31\ \Omega$$

The potential difference across R_{eq} is the same as before $\mathcal{E} = 15\text{ V}$. Thus,

$$I' = \frac{\Delta V'}{R'_{\text{eq}}} = \frac{\mathcal{E}}{R'_{\text{eq}}} = \frac{15\text{ V}}{31\ \Omega} = 0.4839\text{ A}$$

Therefore, the potential difference across the $20\ \Omega$ resistor is


$$\Delta V'_{20} = I'R = (0.4839\text{ A})(20\ \Omega) = 9.68\text{ V}$$

That is, the potential difference across the $20\ \Omega$ resistor is reduced from 10 V to 9.68 V due to the internal resistance of $1\ \Omega$ of the battery. The percentage change in the potential difference is

$$\left(\frac{10.0\text{ V} - 9.68\text{ V}}{10.0\text{ V}} \right) \times 100\% = 3.2\%$$

31.22. Model: The connecting wires are ideal with zero resistance.

Solve:

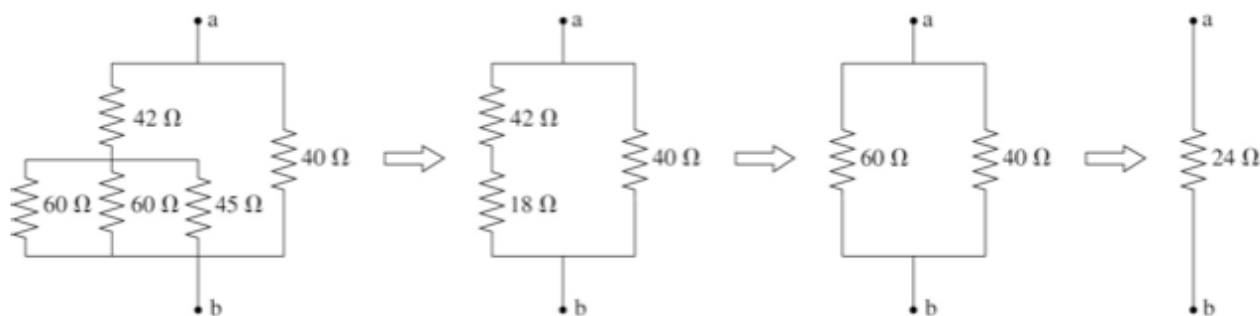

For the first step, the two $60\ \Omega$ resistors and the $45\ \Omega$ resistor are in parallel. Their equivalent resistance is

$$\frac{1}{R_{\text{eq } 1}} = \frac{2}{60\ \Omega} + \frac{1}{45\ \Omega} = \frac{5}{90}\ \Omega \Rightarrow R_{\text{eq } 1} = 18\ \Omega$$

For the second step, resistors $42\ \Omega$ and $R_{\text{eq } 1} = 18\ \Omega$ are in series. Therefore,

$$R_{\text{eq } 2} = R_{\text{eq } 1} + 42\ \Omega = 18\ \Omega + 42\ \Omega = 60\ \Omega$$


For the third step, the resistors $40\ \Omega$ and $R_{\text{eq } 2} = 60\ \Omega$ are in parallel. So,

$$\frac{1}{R_{\text{eq } 3}} = \frac{1}{60\ \Omega} + \frac{1}{40\ \Omega} \Rightarrow R_{\text{eq } 3} = 24\ \Omega$$

The equivalent resistance of the circuit is $24\ \Omega$.

31.23. Model: The connecting wires are ideal with zero resistance.

Solve:

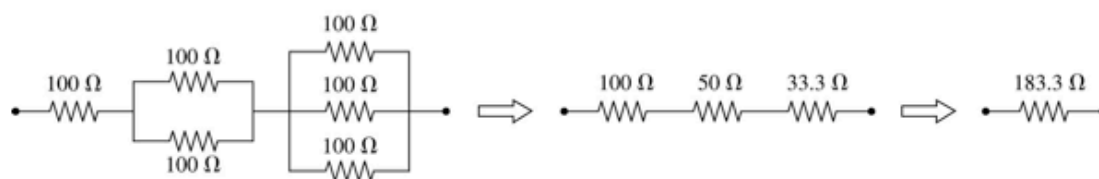

For the first step, the two resistors in the middle of the circuit are in parallel, so their equivalent resistance is

$$\frac{1}{R_{\text{eq } 1}} = \frac{1}{100 \, \Omega} + \frac{1}{100 \, \Omega} \Rightarrow R_{\text{eq } 1} = 50 \, \Omega$$

The three $100 \, \Omega$ resistors at the end are in parallel. Their equivalent resistance is

$$\frac{1}{R_{\text{eq } 2}} = \frac{1}{100 \, \Omega} + \frac{1}{100 \, \Omega} + \frac{1}{100 \, \Omega} \Rightarrow R_{\text{eq } 2} = 33.3 \, \Omega$$


For the second step, the three resistors are in series, so their equivalent resistance is

$$100 \, \Omega + 50 \, \Omega + 33.3 \, \Omega = 183 \, \Omega$$

The equivalent resistance of the circuit is $183 \, \Omega$.

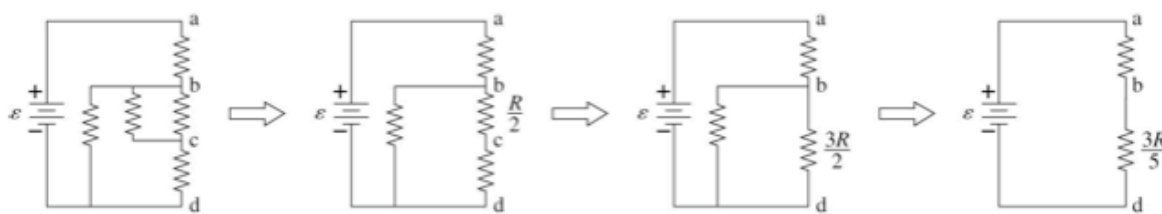31.35. Model: Assume ideal wires.

Visualize: The following equivalent circuits will be useful, where we have labeled three points in the circuits a, b, and c. The unlabeled resistors all have resistance R .



Solve: Because the bulbs are identical, they all have the same resistance, which we shall call R . The bulb brightness is proportional to the power $P = V^2/R$, so we shall calculate the voltage difference across each bulb. First, we find the potential at points a, b, and c with respect to point d (i.e., the negative terminal of the battery), which we shall assign as the zero of the potential. The potential at point a is ε , so $V_a = \varepsilon$. Considering the last equivalent circuit above, we see that the current flowing around the circuit is

$$I = \frac{V_a}{R + 3R/5} = \frac{5\varepsilon}{8R}$$

Therefore, the potential at point b is

$$V_b = V_a - IR = \varepsilon - \frac{5\varepsilon}{8} = \frac{3\varepsilon}{8}$$

Considering the second-to-last circuit, we see that the current flowing from point b to point d must be

$$I_R = \frac{V_b}{3R/2} = \frac{2}{3R} \frac{3\varepsilon}{8} = \frac{\varepsilon}{4R}$$

so, looking at the second circuit, we can find the potential at point c:

$$V_c = V_b - I_R \left(\frac{R}{2} \right) = \frac{3\varepsilon}{8} - \left(\frac{\varepsilon}{4R} \right) \left(\frac{R}{2} \right) = \frac{\varepsilon}{4}$$

In the following table, we put the bulbs and the potential difference across them:

Bulb	Potential Difference	Power
P	$\Delta V = V_b - V_a = -\frac{5\varepsilon}{8}$	$\frac{25}{64} \frac{\varepsilon^2}{R}$
Q	$\Delta V = V_d - V_b = -\frac{3\varepsilon}{8}$	$\frac{9}{64} \frac{\varepsilon^2}{R}$
R	$\Delta V = V_c - V_b = -\frac{\varepsilon}{8}$	$\frac{1}{64} \frac{\varepsilon^2}{R}$
S	$\Delta V = V_c - V_b = -\frac{\varepsilon}{8}$	$\frac{1}{64} \frac{\varepsilon^2}{R}$
T	$\Delta V = V_d - V_c = -\frac{\varepsilon}{4}$	$\frac{4}{64} \frac{\varepsilon^2}{R}$

Thus, ordering the bulbs from brightest to dimmest gives

$$P > Q > T > R = S$$

so the response is D.