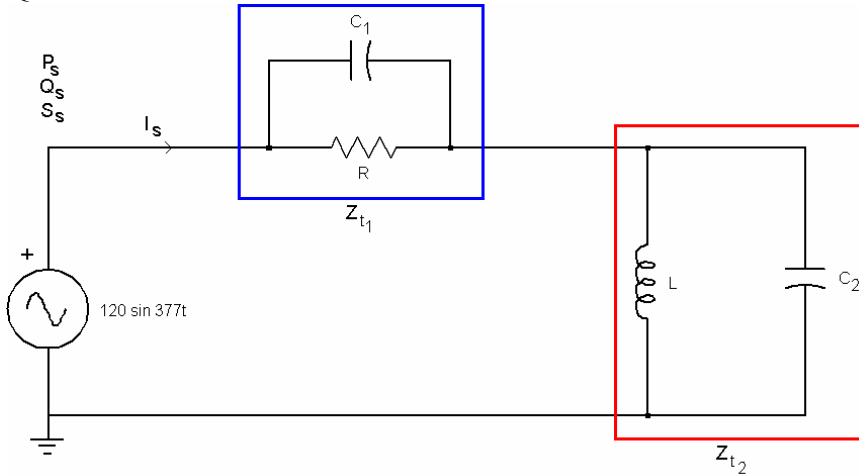


Question



Given:
 $L = 10\text{mH}$
 $R = 10\Omega$
 $C_1 = 100\mu\text{F}$
 $C_2 = 50\mu\text{F}$

1. Calculate: I_s , P_s , Q_s , and S_s ?
2. What is the power factor?
3. Sketch the phasor diagram?

Answer

1.

$$Z_{t_1} = Z_{c_2} // Z_R$$

$$Z_{t_1} = \frac{\left[\frac{1}{j(377)(50)(10^{-6})} \times j(377)(10)(10^{-3}) \right]}{\left[\frac{1}{j(377)(50)(10^{-6})} + j(377)(10)(10^{-3}) \right]} = \frac{200}{-j50} = j4$$

$$Z_{t_2} = Z_{c_1} // Z_R$$

$$Z_{t_2} = \frac{\left[\frac{1}{j(377)(100)(10^{-6})} \times (10) \right]}{\left[\frac{1}{j(377)(100)(10^{-6})} + (10) \right]} = \frac{-j265.252}{10 - j26.5252} = 8.755 - j3.3$$

$$Z_t = Z_{t_1} + Z_{t_2} = j4 + 8.755 - j3.3 = 8.755 + j0.7 = 8.783 \angle 4.57^\circ$$

$$I_s \angle \theta^\circ = \frac{V_s}{Z_t} = \frac{120 \angle 0^\circ}{8.783 \angle 4.57^\circ} = 13.66 \angle -4.57^\circ$$

$$P_s = |V_s| \cdot |I_s| \cdot \cos\theta = 120 \times 13.66 \times \cos(-4.57) = \mathbf{1634\text{W}}$$

$$Q_s = |V_s| \cdot |I_s| \cdot \sin\theta = 120 \times 13.66 \times \sin(-4.57) = \mathbf{-130.67\text{VAR}}$$

$$S_s = |V_s| \cdot |I_s| = 120 \times 13.66 = \mathbf{1639\text{VA}}$$

$$2. \text{P.F.} = \cos\theta = \cos(-4.57) = \mathbf{0.996}$$

3. Phasor Diagram:

