

# ANALOG OUTPUT SYSTEMS

---

## EE3232 DIGITAL SYSTEMS III CLASS NOTES CHAPTER 7

Department of Electrical Engineering  
University of New Brunswick

© C.P. Diduch

January 5, 2000

### SUMMARY

---

- Objectives.
- Quantization and coding.
- Op-amp circuits.
- DAC components.
- DAC transfer functions.
- Weighted resistor DAC.
- R-2R ladder DAC.
- DAC coding (binary, complementary binary, offset binary, complementary offset binary, two's complement).
- DAC specifications.
- DAC calibration.
- Interfacing m-bit DAC's to an n-bit system bus.
- Interfacing the DAC667.
- Sample hold devices.
- Multiplexed sample hold devices.
- Multi-channel analog output systems.

### OBJECTIVES

---

- Using basic components construct weighted resistor and R-2R ladder digital to analog converters, or DAC's.
- To relate DAC hardware and DAC coding.
- Develop H/W and S/W to convert data from one coding to another.

- To develop H/W and S/W for interfacing DAC's to a system bus.
- To develop a procedure and circuit for nulling DAC gain and offset errors.
- To develop the H/W and S/W for interfacing multi-channel output systems to a system bus.

### QUANTIZATION AND CODING


---

- Physical phenomena are **continuous** or analog in nature.
- To interact with the physical world we need to transform
  - From the **discrete domain** of the computer
  - To the **continuous domain** of the real world.
- The transformation uses **digital to analog converters**.
- Only a finite number of values for the physical phenomena can be uniquely represented by an n-bit register.
- The physical phenomena is said to be **quantized** to n-bits, i.e., there are  $2^n$  quanta.
- Each quanta is related to the physical world by some form of coding, i.e., binary, 2's complement ...
 
### OP-AMP CIRCUITS

---

- The fundamental building block of a DAC is the **op-amp**.
- **Op-amps** : characterized by very large gain and very high input impedance.




$$v_o = K (v_+ - v_-)$$

$$K \rightarrow \infty, \quad i \rightarrow 0$$
 
## OP-AMP CIRCUITS (CONT'D)

- An op-amp configured as a (negative gain) **amplifier**.  $v_o$  ?




$$\frac{v_i - v_-}{R_i} = \frac{v_- - v_o}{R_f}, \quad v_- \approx 0$$

$$v_o = -\frac{R_f}{R_i} v_i$$
 
## OP-AMP CIRCUITS (CONT'D)


- An op-amp configured as a **summer**.  $v_o$  ?



$$v_o = -\frac{R_f}{R_1} v_1 - \frac{R_f}{R_1} v_2 \dots - \frac{R_f}{R_N} v_N$$

 
## OP-AMP CIRCUITS (CONT'D)

- An op-amp configured as a high (input) impedance **unity gain amplifier**.  $v_o$  ?



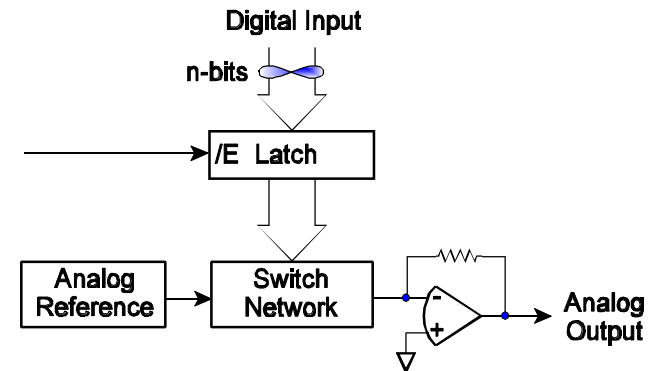
## DAC COMPONENTS

- A DAC consists of :
  - A stable analog reference voltage (or current),
  - A switching network of resistors (or capacitors) and
  - An op-amp for summing voltages or currents.
  - Latch to hold the digital input.


 
## DAC TRANSFER FUNCTIONS


- The DC transfer function of a (straight binary) DAC.
- FS : The full scale analog voltage (the reference voltage).



## DAC TRANSFER FUNCTIONS (CONT'D)

- DAC resolution** : refers to the change in DAC output for a change in the least significant bit, LSB, of the input.
- Resolution may be expressed as a ratio or percentage.
- Resolution of a 10-bit DAC : 1 part in 1024 or 0.0977%.
- Resolution of a 14-bit DAC : 1 part in 16384 or 0.00610%.

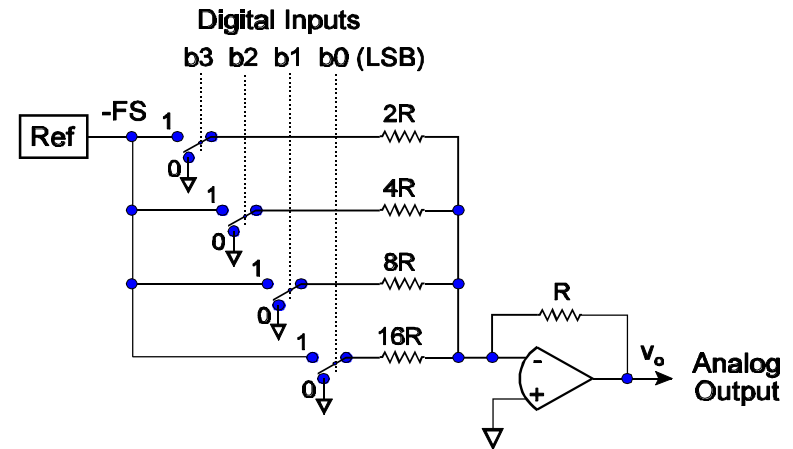
## WEIGHTED RESISTOR (STRAIGHT BINARY) DAC



$$v_o = (b_3 2^3 + b_2 2^2 + b_1 2^1 + b_0 2^0) \Delta$$

$$= B\Delta, \quad \Delta = \frac{FS}{16}, \quad B \text{ unsigned.}$$

## R-2R LADDER (STRAIGHT BINARY) DAC

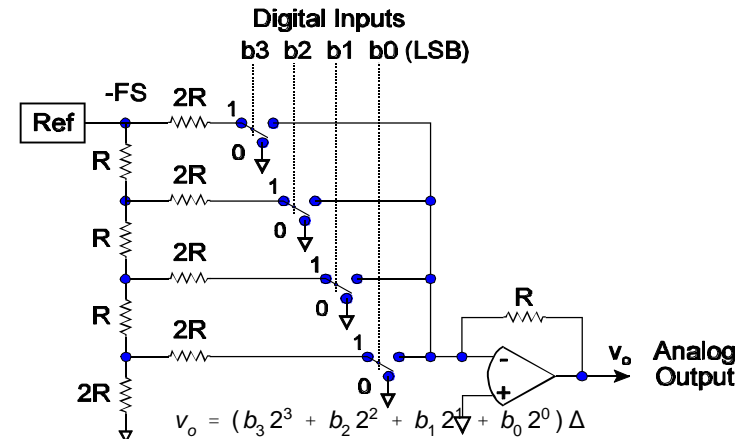


$$v_o = (b_3 2^3 + b_2 2^2 + b_1 2^1 + b_0 2^0) \Delta$$

$$= B\Delta, \quad \Delta = \frac{FS}{16}, \quad B \text{ unsigned.}$$

## DAC CODING

- How do choices in H/W affect coding ?
- Straight Binary (Unipolar).
- Complementary Binary (Unipolar).
- Offset Binary (Bipolar).
- Complementary Offset Binary (Bipolar).
- Two's Complement (Bipolar).


## STRAIGHT BINARY (UNIPOLAR) CODING

 

$$v_o = (b_{n-1} 2^{n-1} + b_{n-2} 2^{n-2} + \dots + b_1 2^1 + b_0 2^0) \Delta$$

$$= B \Delta, \quad \Delta = \frac{FS}{2^n}, \quad B \text{ unsigned.}$$

 
## COMPLEMENTARY BINARY (UNIPOLAR) CODING



$$v_o = (\overline{b_{n-1}} 2^{n-1} + \overline{b_{n-2}} 2^{n-2} + \dots + \overline{b_1} 2^1 + \overline{b_0} 2^0) \Delta$$

$$= \overline{B} \Delta, \quad \Delta = \frac{FS}{2^n}, \quad B \text{ unsigned.}$$

## OFFSET BINARY (BIPOLAR) CODING

 


- For an n-bit DAC,

$$v_{out} = (b_{n-1} 2^{n-1} + b_{n-2} 2^{n-2} + \dots + b_1 2^1 + b_0 2^0) \Delta - \frac{FS}{2}$$

$$= B \Delta - \frac{FS}{2}, \quad \Delta = \frac{FS}{2^n}, \quad B \text{ unsigned.}$$
 
## COMPLEMENTARY OFFSET BINARY (BIPOLAR) CODING




- For an n-bit DAC,

$$v_{out} = (\overline{b_{n-1}} 2^{n-1} + \overline{b_{n-2}} 2^{n-2} + \dots + \overline{b_1} 2^1 + \overline{b_0} 2^0) \Delta - \frac{FS}{2}$$

$$= \overline{B} \Delta - \frac{FS}{2}, \quad \Delta = \frac{FS}{2^n}, \quad B \text{ unsigned.}$$

## TWO'S COMPLEMENT (BIPOLAR) CODING

 

- For an n-bit DAC,

$$v_{out} = (b_{n-1}2^{n-1} + b_{n-2}2^{n-2} + \dots + b_12^1 + b_02^0) \Delta - \frac{FS}{2}$$


$$= B\Delta, \quad \Delta = \frac{FS}{2^n}, \quad B \text{ signed integer.}$$

## BIPOLAR DAC CODING SUMMARY

Digital Coding			Analog Value	
Offset Binary	Complementary Offset Binary	Two's Complement		
0000 0000 0000	1111 1111 1111	1000 0000 0000	$-10 + 0\Delta =$	$10 - 4096\Delta = -2048\Delta$
0000 0000 0001	1111 1111 1110	1000 0000 0001	$-10 + 1\Delta =$	$10 - 4095\Delta = -2047\Delta$
0000 0000 0010	1111 1111 1101	1000 0000 0010	$-10 + 2\Delta =$	$10 - 4094\Delta = -2046\Delta$
⋮	⋮	⋮	⋮	⋮
0011 1111 1111	1100 0000 0000	1011 1111 1111	$-10 + 1023\Delta =$	$10 - 3073\Delta = -1025\Delta$
0100 0000 0000	1011 1111 1111	1100 0000 0000	$-10 + 1024\Delta =$	$10 - 3072\Delta = -1024\Delta$
0100 0000 0001	1011 1111 1110	1100 0000 0001	$-10 + 1025\Delta =$	$10 - 3071\Delta = -1023\Delta$
⋮	⋮	⋮	⋮	⋮
0111 1111 1111	1000 0000 0000	1111 1111 1111	$-10 + 2047\Delta =$	$10 - 2049\Delta = -1\Delta$
1000 0000 0000	0111 1111 1111	0000 0000 0000	$-10 + 2048\Delta =$	$10 - 2048\Delta = 0$
1000 0000 0001	0111 1111 1110	0000 0000 0001	$-10 + 2049\Delta =$	$10 - 2047\Delta = 1\Delta$
⋮	⋮	⋮	⋮	⋮
1011 1111 1111	0100 0000 0000	0011 1111 1111	$-10 + 3071\Delta =$	$10 - 1025\Delta = 1023\Delta$
1100 0000 0000	0011 1111 1111	0100 0000 0000	$-10 + 3072\Delta =$	$10 - 1024\Delta = 1024\Delta$
1100 0000 0001	0011 1111 1110	0100 0000 0001	$-10 + 3073\Delta =$	$10 - 1023\Delta = 1025\Delta$
⋮	⋮	⋮	⋮	⋮
1111 1111 1101	0000 0000 0010	0111 1111 1101	$-10 + 4093\Delta =$	$10 - 3\Delta = 2045\Delta$
1111 1111 1110	0000 0000 0001	0111 1111 1110	$-10 + 4094\Delta =$	$10 - 2\Delta = 2046\Delta$
1111 1111 1111	0000 0000 0000	0111 1111 1111	$-10 + 4095\Delta =$	$10 - 1\Delta = 2047\Delta$

 
## DAC SPECIFICATIONS

- DAC Settling Time:**  $t_s$ , is the (maximum) time required for the analog output of the DAC to settle (within usually 90% of the expected change) when the DAC input changes.



 
## DAC SPECIFICATIONS (CONT'D)

- Real DAC's are characterized by various of phenomena that cause deviations from an ideal DAC,
  - Offset Error,
  - Scale Factor or Gain Error,
  - Nonlinearity Error.


 
## DAC CALIBRATION

- Upper bounds on errors are given in device specs.
- If nonlinear errors are negligible then the offset and gain errors may be zeroed using the circuit and steps below.




- Apply Digital Input for  $v_o = 0$  ideally. Adjust P until  $v_{out} = 0$ .
- Apply Digital Input for  $v_o = v_{max}$  ideally. Adjust  $\delta$  until  $v_{out} = v_{max}$ .

## INTERFACING M-BIT DAC'S TO AN N-BIT DATA BUS

 
### Case (i) $M \leq N$

- The DAC is interfaced to a parallel output port.
- Many DAC's have built-in latches, allowing a direct interface to a system bus.
- The software interface should ensure that time between writing new values to the DAC is  $>$  the DAC settling time.



 
### Case (ii) $M > N$

- Glitches at the DAC output are eliminated if all m-bits are transferred to the DAC simultaneously.
- Requires a **double buffered** configuration (when  $M > N$ ).
- Write x-bits to DBUFF first then write y-bits to DAC.



## INTERFACING THE DAC667

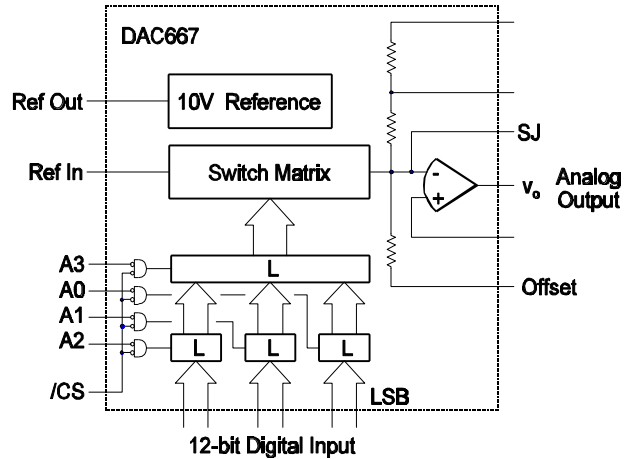


## INTERFACING THE DAC667 (CONT'D)


- Show how to interface the DAC667 to a system bus such that a word is transferred to the DAC as follows,
  - ▶ A write to PortA latches the 8-MSB's of the 12-bit data sent to the DAC (in a double buffer).
  - ▶ A write to PortB latches the 4-LSB's (left justified) and simultaneously loads the 8-MSB's into the DAC.
- The DAC is configured for unipolar +5 FS operation.
- Refer to the data sheets for the DAC667 in your Lab Manual.

## SAMPLE HOLD OR SH DEVICES

- Analogous to an *analog* flip flop.

 


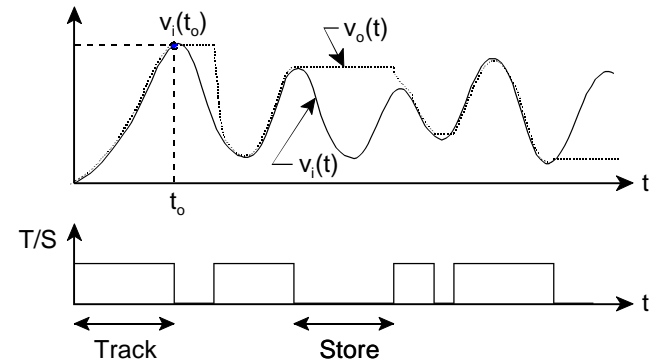- SH Operation
  - ▶ When T/S = '1', Tx is ON  $\therefore v_o(t) = v_i(t)$ .  $v_o(t)$  is said to track or sample  $v_i(t)$ .
  - ▶ When T/S = '0', at  $t = t_0$ , Tx is OFF  $\therefore v_o(t) = v_c(t) = v_i(t_0)$ .  $v_o(t)$  is said to store or hold the value  $v_i(t_0)$ .


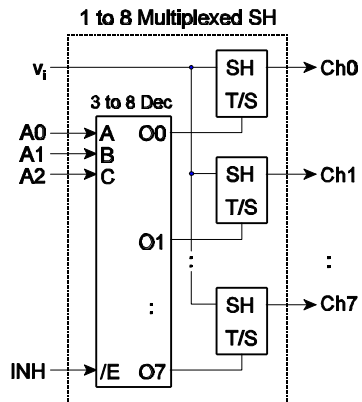
## MULTIPLEXED SAMPLE HOLD DEVICES

- To store (or hold) a new analog value at Ch y
  - Activate INH ← '1' ; (Initially)
  - Apply channel number, y, to A2:0 ;
  - INH ← '0' ;
  - Ch y now tracks  $v_i$ .
  - Activate INH ← '1' ;
  - Ch y holds value.



- Operation,
  - Write INH = active '1' to port PCHS.
  - Write data to port PDAC.
  - Write SH channel number, y, to port PCHS.
  - Write INH = inactive '0' to port PCHS. (Ch y tracks  $v_o$ )

## MULTI-CHANNEL ANALOG OUTPUT SYSTEMS

